
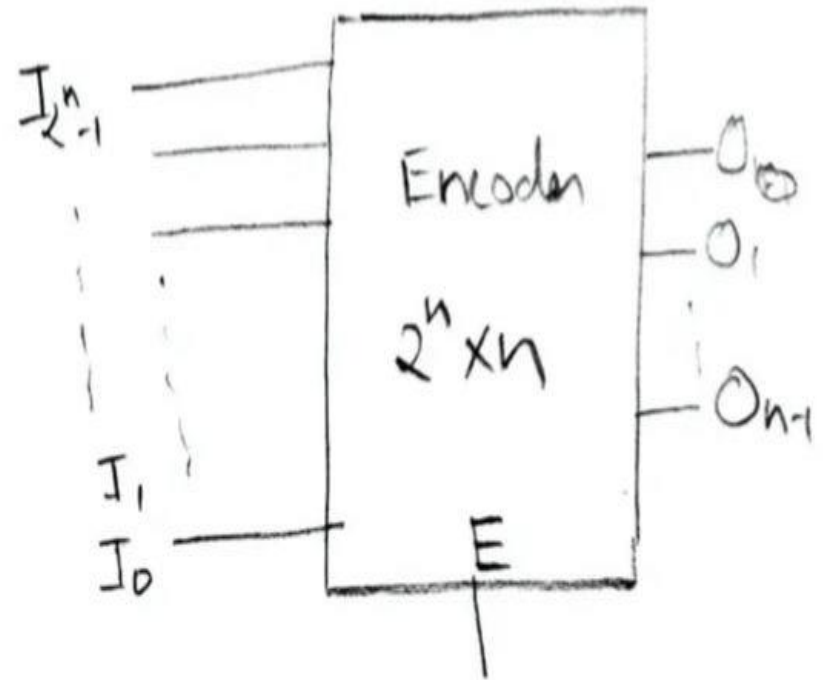


Encoder

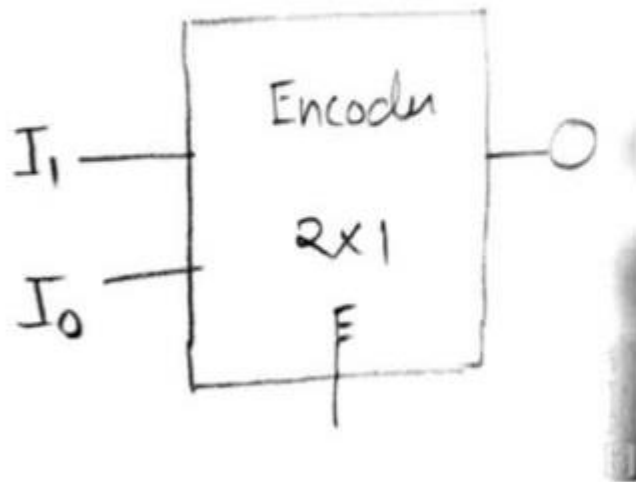- An encoder is a combinational circuit that encode binary information form one of a 2^N input lines and encode it into N output lines, which represent N bit code for the input.
- For simple encoders, it is assumed that only one input line is active at a time.
- Encoder performs the inverse operation of a decoder.




2-to-1 Encoder



I_1	I_0	O_0
0	1	0
1	0	1


4-to-2 Encoder

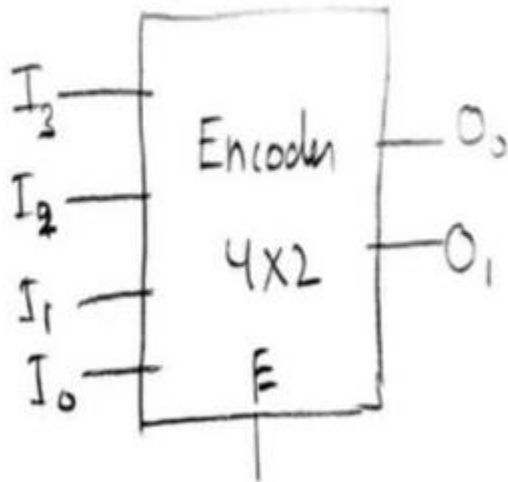

I_3	I_2	I_1	I_0	O_1	O_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

- $O_0 = I_0' I_1' (I_2 \oplus I_3)$
- $O_1 = I_0' I_2' (I_1 \oplus I_3)$

Half Subtractor

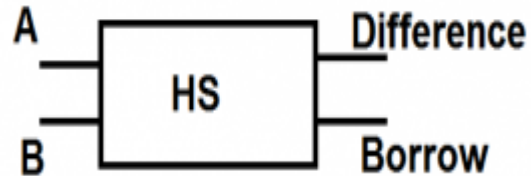


Half Subtractor

Truth Table of Half Subtractor


A	B	Diff	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

Logic Symbol

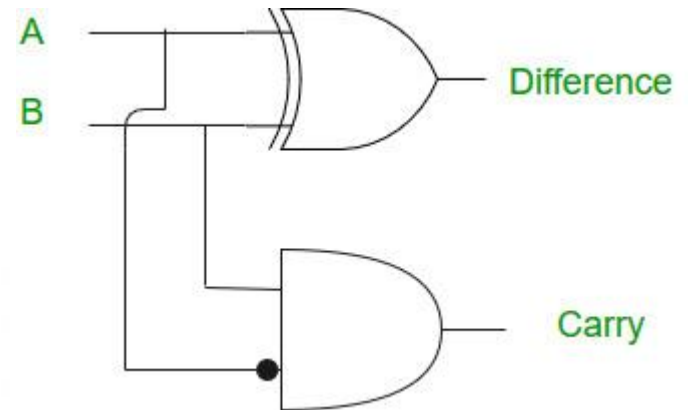

Full Subtractor

A full subtractor is a **combinational circuit** that performs subtraction of two bits, one is minuend and other is subtrahend, taking into account borrow of the previous adjacent lower minuend bit. This circuit **has three inputs and two outputs**. The three inputs A, B and Bin, denote the minuend, subtrahend, and previous borrow, respectively. The two outputs, D and Bout represent the difference and output borrow, respectively.

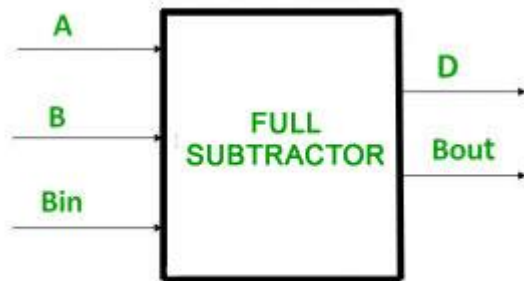

Truth Table

INPUT			OUTPUT	
A	B	Bin	D	Bout
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

From above table we can draw the K-Map as shown for “difference” and “borrow”.

		B Bin			
		00	01	11	10
A	0	0	1	0	1
	1	1	0	1	0

$$D = A'B'Bin + AB'Bin' + A'BBin' + ABBin$$

		B Bin			
		00	01	11	10
A	0	0	1	1	1
	1	0	0	1	0

$$Bout = A'Bin + A'B + BBin$$

Logical expression for difference –

$$\begin{aligned}
 D &= A'B'Bin + A'BBin' + AB'Bin' + ABBin \\
 &= Bin(A'B' + AB) + Bin'(AB' + A'B) \\
 &= Bin(A \text{ XNOR } B) + Bin'(A \text{ XOR } B) \\
 &= Bin(A \text{ XOR } B)' + Bin'(A \text{ XOR } B) \\
 &= Bin \text{ XOR } (A \text{ XOR } B) \\
 &= (A \text{ XOR } B) \text{ XOR } Bin
 \end{aligned}$$

Logical expression for borrow –

$$\begin{aligned} \text{Bout} &= A'B'Bin + A'BBin' + A'BBin + ABBin \\ &= A'B'Bin + A'BBin' + A'BBin + A'BBin + A'BBin + ABBin \\ &= A'Bin(B + B') + A'B(Bin + Bin') + BBin(A + A') \\ &= A'Bin + A'B + BBin \end{aligned}$$

Logic Circuit for Full Subtractor –

