

LESSON PLAN

**SIBSAGAR
POLYTECHNIC,
DEMOW**

**SUBJECT NAME: ELECTRICAL
MEASUREMENT AND
MEASURING INSTRUMENTS I
(EMMI- I)**

SUBJECT CODE: EL- 403

SEMESTER: 4th SEMESTER

Prepared By
PALLABI GOGOI

Department Of Electrical
Engineering

DATE:25.04.2020

CHAPTER 5: POTENTIOMETERS

INTRODUCTION


A potentiometer is an instrument designed to measure an unknown voltage by comparing it with a known voltage. The known voltage may be supplied by a standard cell or any other known voltage reference source. Measurements using comparison methods are capable of a high degree of accuracy because the result obtained does not depend upon the actual deflection of a pointer, as is the case in deflectional methods, but only upon the accuracy with which the voltage of the reference source is known. Another advantage of the potentiometers is that since a potentiometer makes use of a balance or null condition, no current flows and hence no power is consumed in the circuit containing the unknown emf when the instrument is balanced. Thus the determination of voltage by a potentiometer is quite independent of the source resistance.

Since a potentiometer measures voltage, it can also be used to detect current simply by measuring the voltage drop produced by the unknown current passing through a known standard resistance.

The potentiometer is extensively used for a calibration of voltmeters and ammeters and has in fact become the standard for the calibration of these instruments. For the above mentioned advantages the potentiometer has become very important in the field of electrical measurements and calibration.

Basic Potentiometer Circuit: (33rd hour)

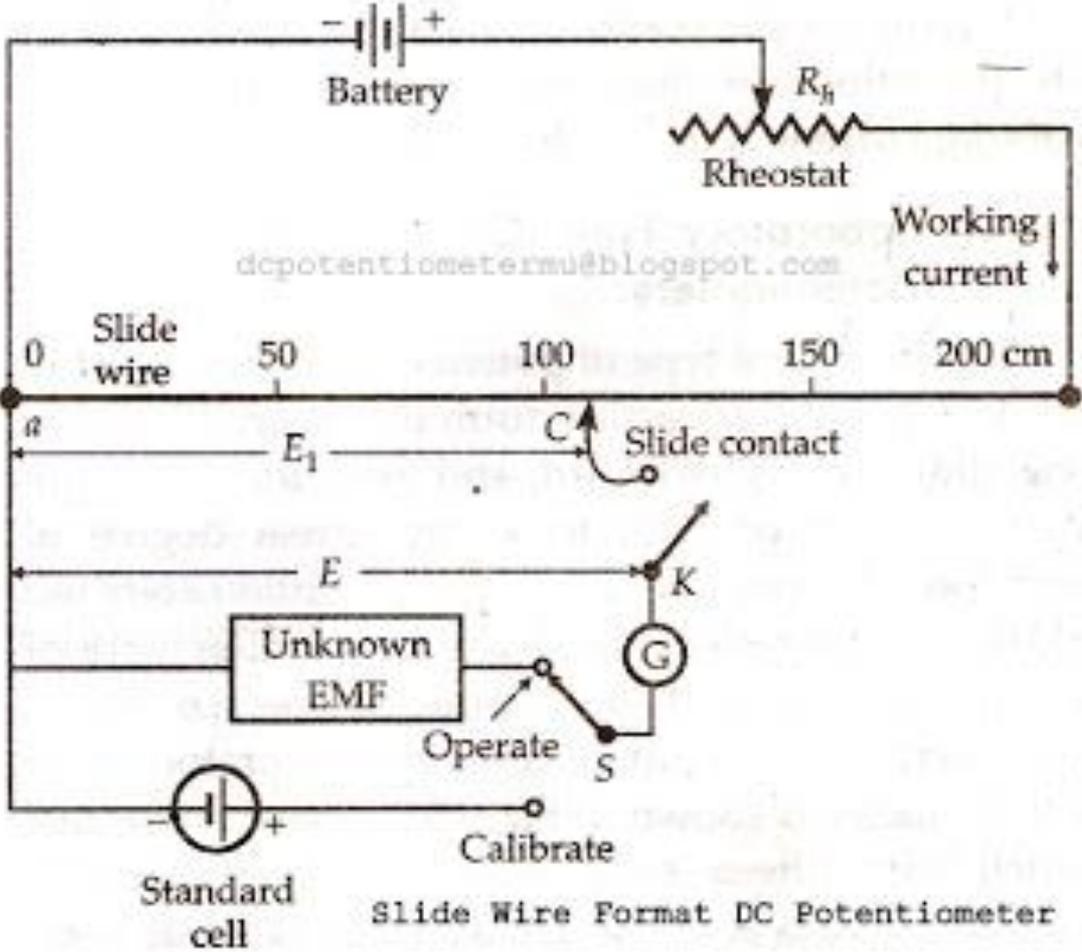The principle of operation of all potentiometers is based on the circuit , which shows the schematic diagram of the basic slide wire potentiometer.



WORKING

With switch 'S' in the "operate" position and the galvanometer key K open, the battery supplies the "working current" through the rheostat R and the slide wire. The working current through the slide wire may be varied by changing the rheostat setting. The method of measuring the unknown voltage, E , depends upon finding a position for the sliding contact such the galvanometer shows zero deflection, i.e., indicates null condition, when the galvanometer key, K, is closed. Zero galvanometer deflection or a null means that the unknown voltage, E , is equal to the voltage drop E_1 across portion ac of the slide wire. Thus determination of the value of unknown voltage now becomes a matter of evaluating the voltage drop E_1 along the portion ac of the slide wire.

The slide wire has a uniform cross-section and hence uniform resistance along its entire length. A calibrated scale in cm and fractions of cm, is placed along the slide wire so that the sliding contact can be placed accurately at any desired position along the slide wire. Since the resistance of slide wire is known accurately, the voltage drop along the slide wire can be controlled by adjusting the value of working current. The process of adjusting the working current so as to match the voltage drop across a portion of sliding wire against a standard reference source is known as "Standardisation".

Standardisation: (34th hour)

The procedure for standardisation of the potentiometer is illustrated by the following example:

The slide wire of Fig. 15.1 has a total length of 200 cm and a resistance of 200 Ω . The emf of the standard cell is 1.0186 V. Switch 'S' is thrown to "calibrate" position and the sliding contact is placed at 101.86 cm mark on the slide wire scale.

The rheostat R_h is now adjusted so as to vary the working current. This adjustment is carried on till the galvanometer shows no deflection when key 'K' is pressed.

Under these conditions, the voltage drop along the 101.86 cm portion of the slide wire is equal to standard cell voltage of 1.0186 V. Since the 101.86 cm portion of the slide wire has a resistance of 101.86 Ω , the working current in fact has been adjusted to a value ;

$$1.0186 \times 1000 = 10 \text{ mA. } 101.86$$

The voltage at any point along the slide wire is proportional to the length of slide wire. This voltage is obtained by converting the calibrated length into the corresponding voltage, simply by placing the decimal point in the proper position e.g. 153.6 cm. = 1.536 V. If the potentiometer has been calibrated once, its working current is never changed.